

Finite State Machines

CS 350: Computer Organization & Assembler Language Programming

A. Why?

- Finite state machines are a common model for simple programs over fixed memory.

B. Outcomes

After this lecture, you should know

- What makes up a finite state machine (FSM) and how they execute.
- How to translate between FSMs state transition diagrams and tables and how to use them to trace FSM execution.

C. Finite State Machines

- One way to describe sequential computations uses **finite state machines (FSMs)**.
 - An FSM takes a sequence of symbols as input.
 - Different kinds of FSMs have different outputs.
 - The simplest kind of FSM is a **recognizer**: It just says “Yes” or “No” at the end of input.
 - The FSM **accepts** the input if it says “Yes,”
 - The FSM **rejects** the input if it says “No.”
 - E.g. you can build an FSM that takes a sequence of 0’s and 1’s and accepts strings that include exactly two occurrences of 1.
 - More-complicated FSMs can produce output symbols during the calculation.
- **To specify an FSM** you specify
 - The **state set** (the set of all possible states).
 - The **start state** (the one the FSM begins execution in).

- The set of **accepting states** (when the FSM ends computation, it accepts the input iff it ends in an accepting state).
- A **transition function** that describes how the FSM executes.
- **FSM Implementation**
 - Implement FSM using sequential logic circuit
 - FSM states is unsigned bitstring of some fixed length.
 - An FSM is always in a state (which is why we need a start state).
 - The set of states isn't modifiable during execution.
- **FSM Execution:**
 - Initialize state \leftarrow start state;
while there exists more input {
 read character of input
 set state to new state
 i.e., state \leftarrow transition_function(input_char, state)
}
if state \in Accepting States **then**
 print "Accept"
else
 print "Reject"
- **FSM Transition Function:**
 - The transition function takes an input character and the current state; it produces the next state for the machine (may change the state or stay in the current state).
- **FSM Example:**
 - Machine M_1 will read strings of **a**'s and **b**'s and accept strings that contain exactly two occurrences of **b**.
 - We'll have four states named S_0 , S_1 , S_2 , and S_3 .
 - For $k = 0, 1$, or 2 , we'll be in state S_k iff we've seen exactly k **b**'s.
 - We'll be in state S_3 if we've seen three or more **b**'s.
 - State S_0 is the initial state, state S_2 is the (only) accepting state.

- The transitions:
 - For $k \in \{0, 1, 2\}$, if we're in state S_k and the input is **b**, we go to state S_{k+1} .
 - If we're in state S_3 and the input is **b**, we stay in S_3 .
 - For every state, if we see an **a**, we stay in that state.
- Sample execution
 - One way to describe an execution of an FSM uses two rows.
 - The top row contains the symbols of the input.
 - The bottom row contains the states that the FSM is in as it reads the input.
 - We stagger the columns for visibility
 - Here's a run with input **abaabaa**. Since we end in state S_2 , we accept the input.
 - Note the leftmost column includes no symbol but the state S_0 ; this is how we describe starting in state S_0 .

	a		b		a		a		b		a		a	
S_0		S_0		S_1		S_1		S_1		S_2		S_2		S_2

- (Quick question: What strings would we accept if we change the accepting state from S_2 to S_3 ? What if we make every state accepting *except for* S_2 ?)

D. Representing Transition Functions


- **State Transition Table:** One way to describe a finite state machine's transition function uses a table with three columns:
 - The first two columns list a state and input symbol. The third column lists the state we go to if we see the given state and input symbol.

- **Example:** To the right is a transition table for the machine M_1 above.
 - To get a complete description of M_1 , we must also list the initial state (i.e., S_0) and accepting state(s) (i.e., S_2 .)
- **State Transition Diagram:** The other technique for representing an FSM's state transition function uses a directed graph:
 - Each state is represented as a circle.
 - Each transition is represented as an arc from the old state to the new state, with the arc labelled by the input symbol.
 - The initial state is indicated by drawing an arrow to it but with no source.
 - To indicate that a state is an accepting state, we draw a concentric circle on it.
- (By the way, it's okay for the initial state to be an accepting state, though it doesn't have to be.)

<i>Machine M_1</i>		
<i>State</i>	<i>Input</i>	<i>New State</i>
S_0	a	S_0
S_0	b	S_1
S_1	a	S_1
S_1	b	S_2
S_2	a	S_2
S_2	b	S_3
S_3	a	S_3
S_3	b	S_3


Initial state: S_0 ; Accepting state: S_2

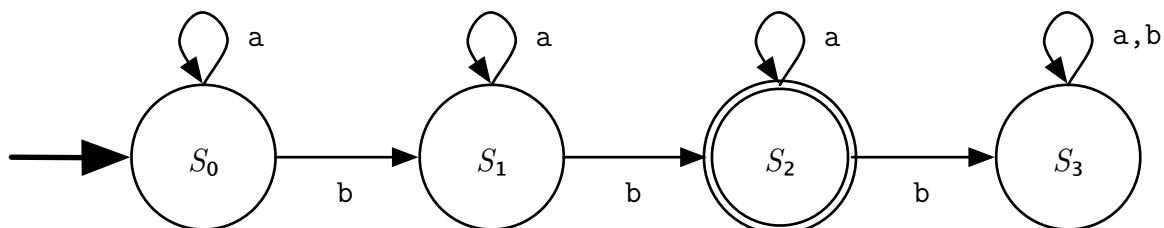- **Example:** Here is a state transition table for the machine M_1 above.



- **Example:** Here's an FSM that reads strings of 0's and 1's and accepts iff the string only contained 0's.

State	Input	New State
No 1's	0	No 1's
No 1's	1	Has 1's
Has 1's	0	Has 1's
Has 1's	1	Has 1's

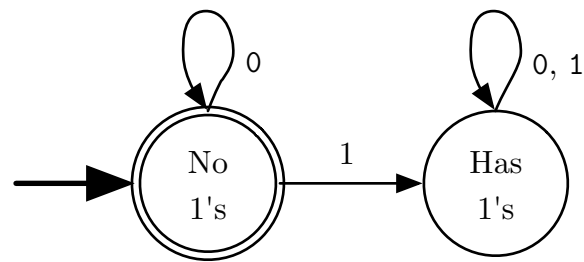


State Table for All-zero recognizer
Start and accepting state: No 1's

State Diagram for All-zero recognizer

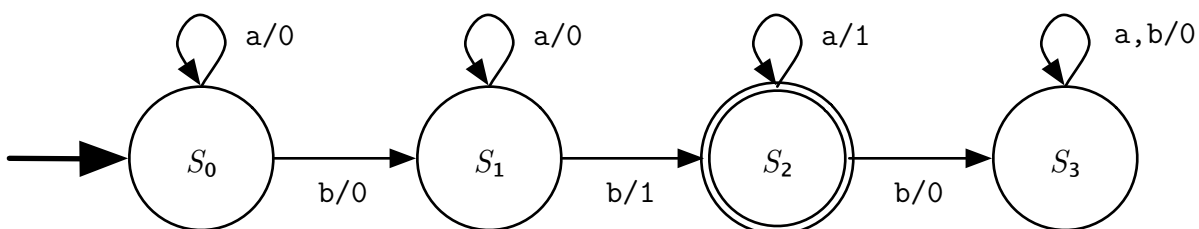E. Finite State Machines With Output

- An FSM with output generates a string of symbols as it processes its input.
- Two kinds of FSMs with outputs
 - A **Mealy machine** associates an output with each transition.
 - With transition table, add another column for the output.
 - With transition diagram, add slash and output to each arc.
 - A **Moore machine** associates an output with each state
 - Add another table mapping states to outputs
- **Example** (output on transition): Let machine M_2 extend M_1 : Output a 1 for the two transitions that lead to S_2 ; output a 0 for the other transitions.
 - With input **abababab**, we output **00011000** .



<i>State</i>	<i>Input</i>	<i>New State</i>	<i>Output</i>
S_0	a	S_0	0
S_0	b	S_1	0
S_1	a	S_1	0
S_1	b	S_2	1
S_2	a	S_2	1
S_2	b	S_3	0
S_3	a	S_3	0
S_3	b	S_3	0

M_2 : A Finite State Machine with Output


Start state: S_0 ; Accepting state: S_2 .

- **Example** (output by state): Let M_3 extend M_1 with output 0 for states S_0 , S_1 , and S_3 ; output 1 for S_2 . With input **abababab**, we get output **00001100**. In the table below, (*) indicates a difference in output from the M_2 machine of the previous example.

<i>State</i>	<i>Output</i>	<i>Input</i>	<i>New State</i>
S_0	0	a	S_0
S_0	0	b	S_1
S_1	0	a	S_1
S_1	0*	b	S_2
S_2	1	a	S_2
S_2	1*	b	S_3
S_3	0	a	S_3
S_3	0	b	S_3

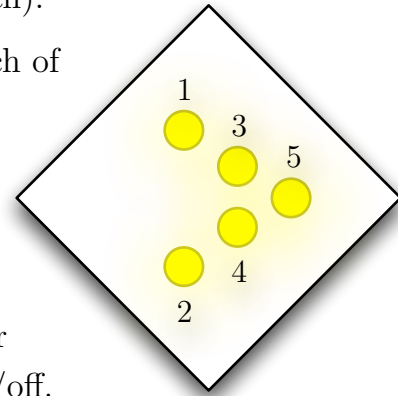
F. Textbook's Flashing Warning Sign Example

- The textbook's flashing warning sign example associates outputs with states.
 - The sign has **one bit of input** (an on/off switch).
 - It has **two bits of memory** (to remember which of four states we're in).
 - It has five outputs, one bit each, to control five lights.
 - But actually, we can get by with **three outputs**, one for (**Lights 1 & 2**) on/off, one for (**Lights 3 & 4**) on/off, and one for **Light 5** on/off.




Light Numbers


- The lights are arranged in a rightward V-shaped arrow.
- For the finite state machine, the input will be the value of the switch S (0 or 1 for off and on). With each clock beat, we check the switch to see if it's on or off, so our input is a sequence of 0s and 1s.
- If the switch is on, the lights cycle as in the states below: 0, 1, 2, 3, 0, 1, 2, 3, etc. If the switch is off, the lights go off and we go to state 0; if we're already in state 0, we keep the lights off and remain in state 0.

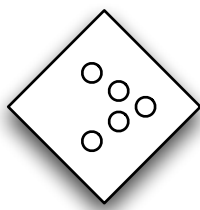


State 0
No Lights On

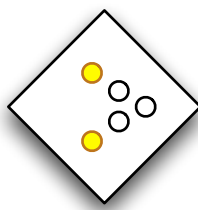

State 1
Lights 1-2 On

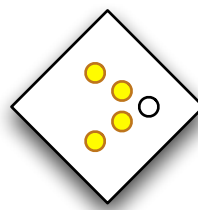


State 2
Lights 1-4 On

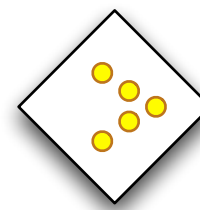

State 3
Lights 1-5 On

State	Lights 1 & 2	Lights 3 & 4	Light 5
00	0	0	0
01	1	0	0
10	1	1	0
11	1	1	1

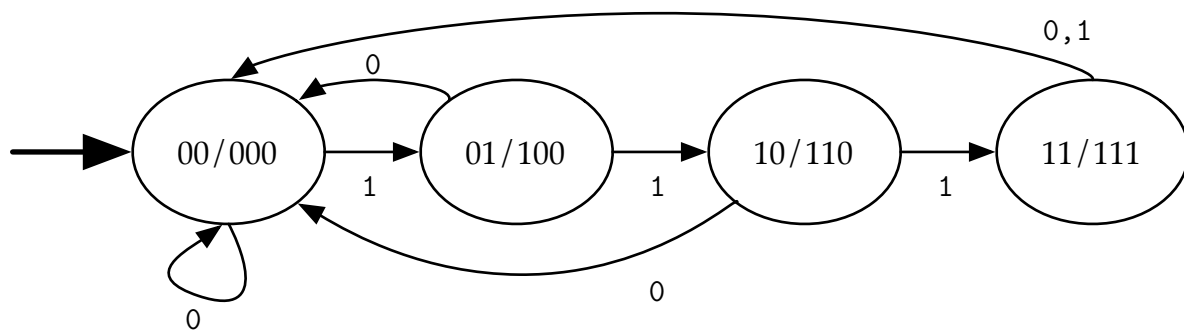
- Here's a state transition diagram: Each state label includes a slash and the three bits of output for that state (Lights 1 & 2, Lights 3 & 4, and Light 5). The arcs are labeled with the input S . There's no accepting state indicated because we only run the machine for its output.



State Transition Diagram for Flashing Warning Sign

- To implement this FSM in hardware, we need to describe the output bits and new state bits using combinatorial equations. In a departure from the book's notation, I'm going to use C for the current state, N for the new state, and L_{12} , L_{34} , and L_5 to indicate whether the indicated lights should be on or off. (Recall bits are numbered from right-to-left, so C = the string $C_1 C_0$ and N = the string $N_1 N_0$.)

$L_{12} = S(C_1 + C_0)$	Lights 1 and 2 are on in states 01, 10, and 11
$L_{34} = S C_1$	Lights 3 and 4 are on in states 10 or 11
$L_5 = S C_1 C_0$	Light 5 is on in state 11
$N_1 = S(C_1 \oplus C_0)$	From states 01 and 10 we go to states 10 and 11
$N_0 = S \overline{C_0}$	From states 00 and 10 we go to states 01 and 11

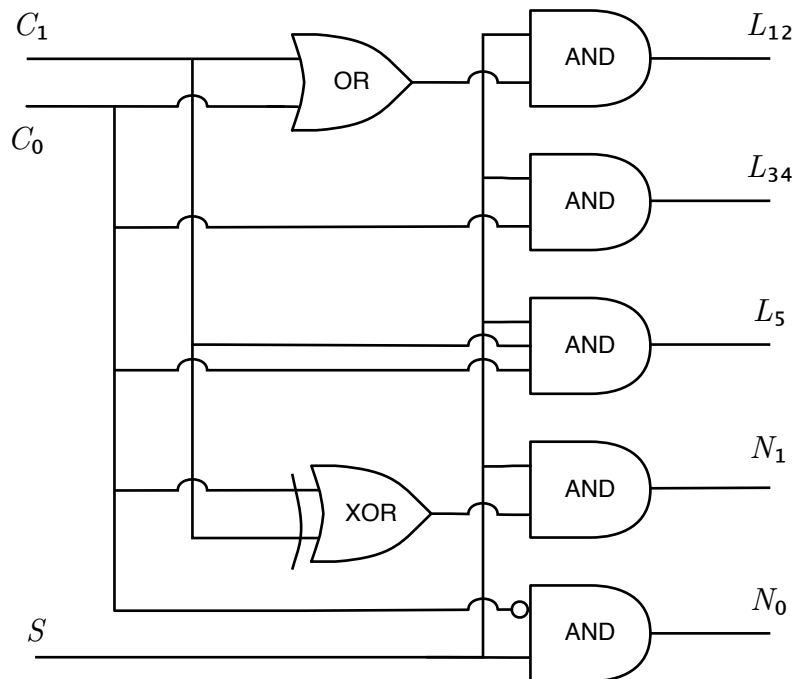

Circuit for Flashing Warning Light

Finite State Machines

CS 350: Computer Organization & Assembler Language Programming

A. Why?

- Finite state machines are a common model for simple programs over a fixed amount of memory.


B. Objectives

At the end of this activity, you should:

- Be able to trace the execution of a finite state machine using its state transition table or state transition diagram.
- Be able to translate a state diagram for a finite state machine to an equivalent state transition table.

C. Questions

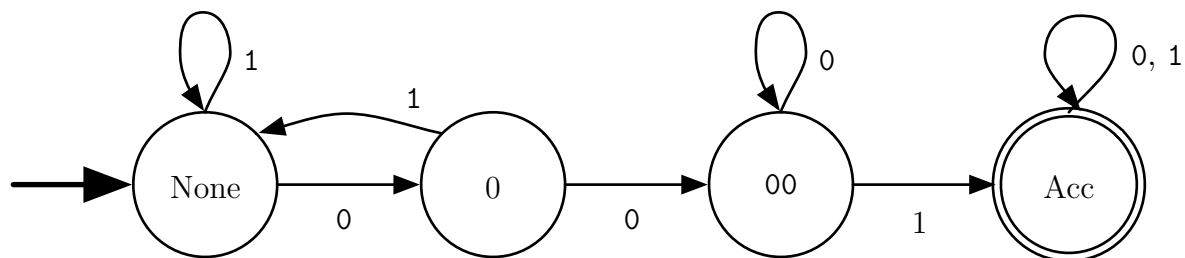1. Here is a the state diagram for a finite state machine.



- (a) Trace the execution of this machine on the input **0100010**.
- (b) What is the pattern of strings accepted by this machine?
- (c) Complete the state transition table below for this machine.

<i>State</i>	<i>Input</i>	<i>New State</i>
None	0	0
None	1	None
0		
0		
00		
00		
Acc		
Acc		

- We'd like a finite state machine that takes an input string of 0's and 1's and has two states *E* and *O* (for even and odd), which it uses to keep track of whether the input has an even or odd number of 0's. It accepts strings with even numbers of 0's. (a) Draw a state diagram for the machine. (b) Give a state transition table for the machine.
- Fill in the following trace of execution table for the flashing warning sign FSM.

<i>C</i>₁ (State hi bit)	0	0						
<i>C</i>₀ (State low bit)	0	0						
<i>S</i> (On-Off Switch)	0	1	1	1	1	1	0	0
<i>L</i>₁₂ (Lights 1, 2)	0	0						
<i>L</i>₃₄ (Lights 3, 4)	0	0						
<i>L</i>₅ (Light 5)	0	0						
<i>N</i>₁ (new <i>C</i>₁)	0	0						
<i>N</i>₀ (new <i>C</i>₀)	0	1						

Solution

1a. (Execution trace):


	0	1		0	0	0	1	1	0
None	0	None	0	00	00	Acc	Acc	Acc	

1b. It accepts any string that contains a **001**

1c. (Transition table): Initial state: “None”; accepting state: Acc.

<i>State</i>	<i>Input</i>	<i>New State</i>
None	0	0
None	1	None
0	0	00
0	1	None
00	0	00
00	1	Acc
Acc	0	Acc
Acc	1	Acc

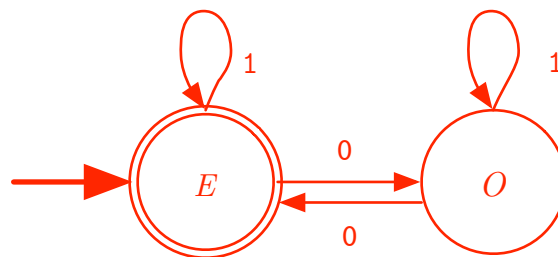2a. Note that since we’re tracking only the **0**’s, the **1**’s don’t change the state. Each **0** changes the state from even to odd (or vice versa).



2b. Initial and accepting state: E

<i>State</i>	<i>Input</i>	<i>New State</i>
E	0	O
E	1	E
O	0	E
O	1	O

3. Output and transition table:

C_1 (State hi bit)	0	0	0	1	1	0	0	0
C_0 (State low bit)	0	0	1	0	1	0	1	0
S (On-Off Switch)	0	1	1	1	1	1	0	0
L_{12} (Lights 1 & 2)	0	0	1	1	1	0	1	0
L_{34} (Lights 3 & 4)	0	0	0	1	1	0	0	0
L_5 (Light 5)	0	0	0	0	1	0	0	0
N_1 (new C_1)	0	0	1	1	0	0	0	0
N_0 (new C_0)	0	1	0	1	0	1	0	0